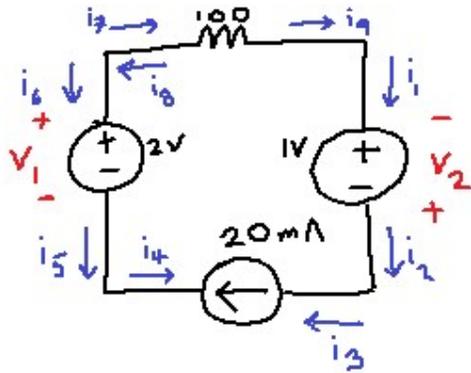


Find voltages and currents marked in the figure.



Write your answers in the following format:

- Q2.1.  $V_1 = 0V$
- Q2.2.  $V_2 = 0V$
- Q2.3.  $I_1 = 0.01A$
- Q2.4.  $I_2 = 0.01A$
- Q2.5.  $I_3 = 0.01A$
- Q2.6.  $I_4 = 0.01A$
- Q2.7.  $I_5 = -0.01A$
- Q2.8.  $I_6 = -0.01A$
- Q2.9.  $I_7 = -0.01A$
- Q2.10.  $I_8 = -0.01A$
- Q2.11.  $I_9 = -0.01A$