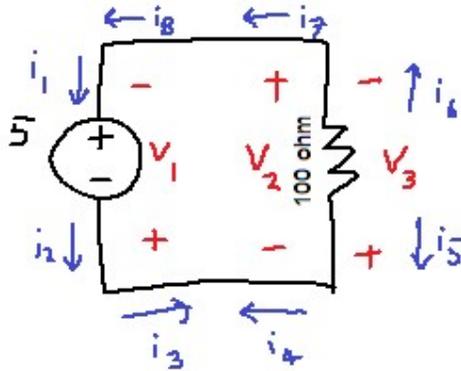


Find voltages and currents marked in the figure.



Write your answers in the following format:

- Q1.  $V_1 = 0V$
- Q2.  $V_2 = 0V$
- Q3.  $V_3 = 0V$
- Q4.  $I_1 = 0.8A$
- Q5.  $I_2 = 0.8A$
- Q6.  $I_3 = 0.8A$
- Q7.  $I_4 = 0.8A$
- Q8.  $I_5 = -0.8A$
- Q9.  $I_6 = -0.8A$
- Q10.  $I_7 = -0.8A$
- Q11.  $I_8 = -0.8A$