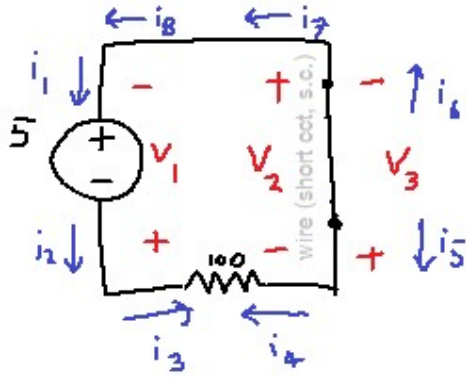


Find voltages and currents marked in the figure.



Write your answers in the following format:

- Q1. $V_1 = -5V$
- Q2. $V_2 = 0V$
- Q3. $V_3 = 0V$
- Q4. $I_1 = 0.8A$
- Q5. $I_2 = 0.8A$
- Q6. $I_3 = 0.8A$
- Q7. $I_4 = 0.8A$
- Q8. $I_5 = -0.8A$
- Q9. $I_6 = -0.8A$
- Q10. $I_7 = -0.8A$
- Q11. $I_8 = -0.8A$