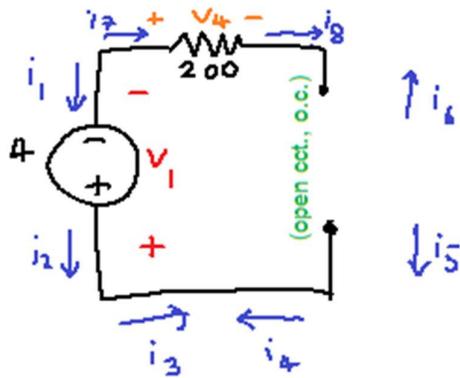


Find voltages and currents marked in the figure.



Write your answers in the following format:

- Q.  $V_1 = 1V$
- Q.  $V_4 = 1V$
- Q.  $I_1 = 0.001A$
- Q.  $I_2 = -0.001A$
- Q.  $I_3 = 0.001A$
- Q.  $I_4 = -0.001A$
- Q.  $I_5 = 0.001A$
- Q.  $I_6 = -0.001A$
- Q.  $I_7 = 0.001A$
- Q.  $I_8 = -0.001A$