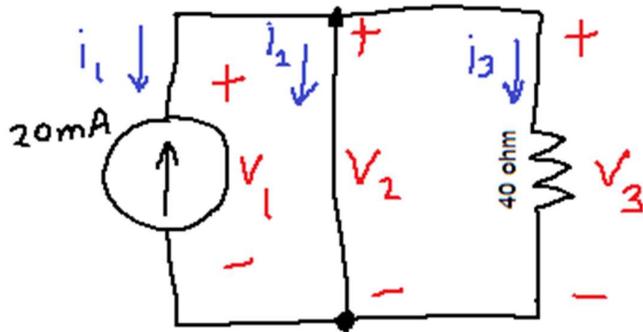


Find voltages and currents marked in the figure.



Write your answers in the following format:

- Q.  $V_1 = 1\text{V}$
- Q.  $V_2 = 1\text{V}$
- Q.  $V_3 = 1\text{V}$
- Q.  $I_1 = 0.1\text{A}$
- Q.  $I_2 = 0.1\text{A}$
- Q.  $I_3 = 0.1\text{A}$