

(a) Write KVL equation for loop marked in the picture. Start from a voltage source and progress along the direction guided by the arrow.


(b) Find  $i_1$ .

(c) Find  $i_2$ .

(d) Find  $v_1$ .

(e) Find  $v_2$ .

(f) Find  $v_x$ .

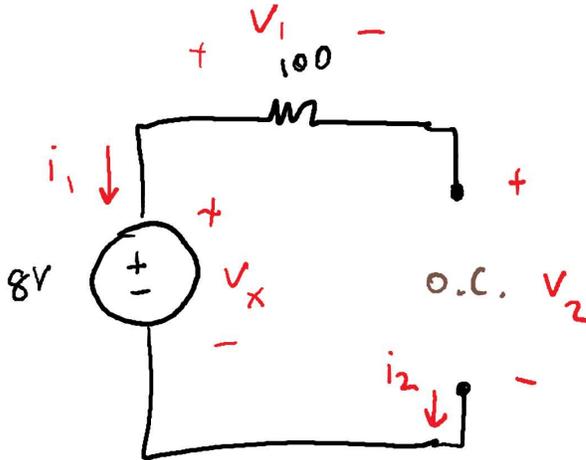

Write your answers in the following format:

Qa:  $10 + 10 i_1 - 10 + 0.1 v_1 + 40 = 0$

Qb.  $i_1 = 0A$

Qc.  $i_2 = 0A$

Qd.  $v_1 = 0V$

Qe.  $v_2 = 0V$

Qf.  $v_x = 0V$