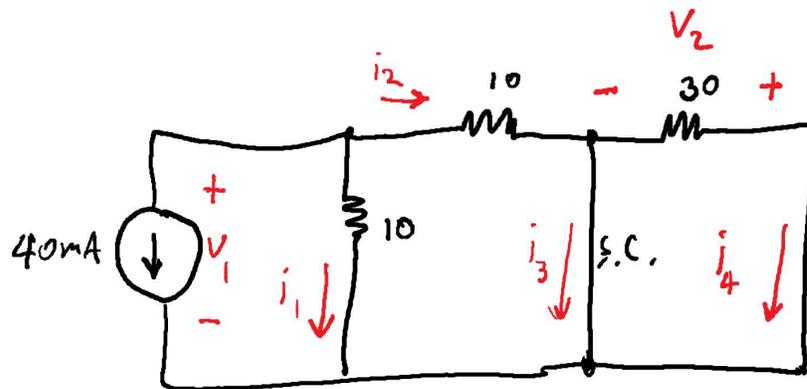


- (a) Find  $i_1$ .
- (b) Find  $i_2$ .
- (c) Find  $i_3$ .
- (d) Find  $i_4$ .
- (e) Find  $v_1$ .
- (f) Find  $v_2$ .



Write your answers in the following format:

- Qa.  $i_1 = 0A$
- Qb.  $i_2 = 0A$
- Qc.  $i_3 = 0A$
- Qd.  $i_4 = 0A$
- Qe.  $v_1 = 0V$
- Qf.  $v_2 = 0V$