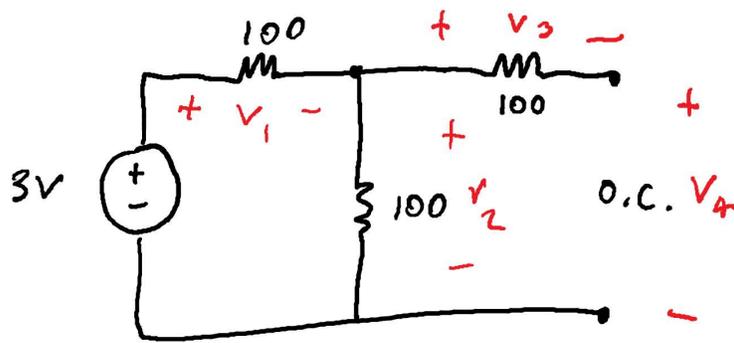


- (a) Find v_1 .
- (b) Find v_2 .
- (c) Find v_3 .
- (d) Find v_4 .



Write your answers in the following format:

Qa. $v_1 = 0V$ Qb. $v_2 = 0V$ Qc. $v_3 = 0V$ Qd. $v_4 = 0V$
--