



Answer the following questions:

Q1. Do nodal analysis by writing the supernode (a-b) equation. Arrange terms in order:  $V_a$  term and then  $V_b$  term on the left and a constant on the right. Manipulate and simplify the equation such that (1) all variables are nodal voltages, (2) the equation is written as a sum of products and (3)  $V_a$  term is positive.

Q2. Solve for  $V_b$ .

Q3. Solve for  $i_1$ .

Write your answers in the following format.

Q1.1:  $0.0 V_a + 0.0 V_b = 0.0$

Q1.2.  $V_b = 0.0 \text{ V}$

Q1.3.  $i_1 = 0.0 \text{ A}$