



Given  $V_s = 10 \cos(2513.27412 t)$ ,  $R = 100 \Omega$ ,  $C = 2 \mu F$ , determine values of the following variables at AC steady state:

- Q1. Magnitude of  $V_s$  in Vpp (peak-to-peak voltage),
- Q2. Frequency of  $V_s$  in Hz,
- Q3. Impedance of resistor  $R$  in ohm,
- Q4. Impedance of capacitor  $C$  in ohm (if it is a complex, write in  $a + j b$  format---there is a space between  $j$  and the imaginary number),
- Q5. Magnitude of current  $i$  in App (peak-to-peak ampere),
- Q6. Frequency of current  $i$  in Hz,
- Q7. Phase  $\theta$  of current  $i$  (with reference to the phase of voltage  $V_s$ ) in radian within range  $(-\pi, \pi]$ ,
- Q8. Phase  $\theta$  in degree within range  $(-180, 180]$ ,
- Q9. Average power  $P_R$  dissipated over resistor  $R$  in watt,
- Q10. Average power  $P_C$  dissipated over capacitor  $C$  in watt.

*Hint: convert  $V_s$  to phasor and use phasor analysis.*

Write your answers in the following format.

Q1.1. magpp\_vs = 0 V  
 Q1.2. freq\_vs = 0 Hz  
 Q1.3. ZR = 0 ohm  
 Q1.4. ZC = 0 ohm  
 Q1.5. magpp\_i = 0 A  
 Q1.6. freq\_i = 0 Hz  
 Q1.7. phase\_i = 0 rad  
 Q1.8. phase\_i = 0 deg  
 Q1.9. PR = 0 W  
 Q1.10. PC = 0 W