



Given the above schematic diagram and V_1 , V_2 and V_3 have the same magnitude of 311V, frequency 50Hz, but different phases 0, 120° , and 240° , respectively. Answer the following questions for AC steady state analysis.

- Q1. Magnitude of nodal voltage $V(h)$.
- Q2. Magnitude of current i_x passing through V_1 from + to -.
- Q3. Phase of current i_x passing through V_1 from + to -.
- Q4. Magnitude of current i_y passing through V_2 from + to -.
- Q5. Phase of current i_y passing through V_2 from + to -.
- Q6. Magnitude of current i_z passing through V_3 from + to -.
- Q7. Phase of current i_z passing through V_3 from + to -.
- Q8. Frequency of i_z in Hz.

Write your answers in the following format.

- A1. $V_h = 0 \text{ V}$
- A2. $\text{Mag } i_x = 0 \text{ A}$
- A3. $\text{Phase } i_x = 0 \text{ rad}$
- A4. $\text{Mag } i_y = 0 \text{ A}$
- A5. $\text{Phase } i_y = 0 \text{ rad}$
- A6. $\text{Mag } i_z = 0 \text{ A}$
- A7. $\text{Phase } i_z = 0 \text{ rad}$

A8. Freq iz = 0 Hz